

# Truth table

even parity

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1 $m_1$
0	0	1	0	1 $m_2$
0	0	1	1	0
0	1	0	0	1 $m_4$
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1 $m_7$
1	0	0	0	1 $m_8$
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1 $m_{11}$
1	1	0	0	0
1	1	0	1	1 $m_{13}$
1	1	1	0	1 $m_{14}$
1	1	1	1	0

# Karnaugh map

CD \ AB	A			
	0	1	2	3
0	0	1	12	1
1	1	5	13	1
2	3	7	15	1
3	2	6	14	1

B

$$ABC\bar{D} + AB\bar{C}D + A\bar{B}CD + A\bar{B}\bar{C}\bar{D} + \bar{A}BCD + \bar{A}B\bar{C}\bar{D}$$

$$+ \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}\bar{C}D$$


$$= AB(C \oplus D) + A\bar{B}(CD + \bar{C}\bar{D}) + \bar{A}B(CD + \bar{C}\bar{D}) + \bar{A}\bar{B}(C \oplus D)$$

$$= AB(C \oplus D) + CD(A \oplus B) + \bar{C}\bar{D}(A \oplus B) + \bar{A}\bar{B}(C \oplus D)$$

$$(A \oplus B)(CD + \bar{C}\bar{D}) + (C \oplus D)(AB + \bar{A}\bar{B})$$

$$= (A \oplus B) \oplus (C \oplus D) = F \text{ (even parity)}$$

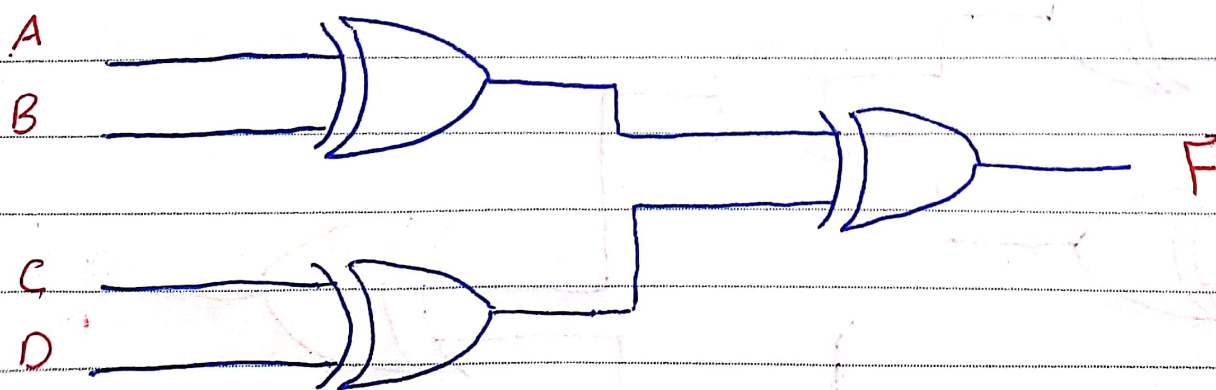Of course, it ~~was~~ possible to write this from the beginning.



expand the circuit to include the odd parity as well.

even ↑ F	even/odd	q
0	0	1
0	1	0
1	0	0
1	1	1

expand the circuit to include the odd parity as well.

even ↑ F	odd/even	q
0	0	0
0	1	1
1	0	1
1	1	0

$$\Rightarrow q = F \oplus \text{odd}$$

